



Connect Shiksha IoT Academy

15-Day IoT & Robotics Program

Transforming Engineering Students into IoT Professionals

Day 4: LDR Sensor + LED Automation using NodeMCU

Step 1: Connect the LDR Sensor

Components Needed:

- 1x LDR
- 1x 10kΩ Resistor
- Breadboard
- Jumper wires
- NodeMCU (ESP8266)

Connections:

- One leg of LDR → **3.3V**
- Other leg of LDR → **A0 (Analog pin)**
- **10kΩ Resistor** → Between LDR's second leg and **GND**

This forms a **voltage divider** that sends analog values to the A0 pin.

Step 2: Read Light Value from LDR

Code:

```
void setup() {  
    Serial.begin(115200); // Start Serial Monitor  
}
```

```
void loop() {  
    int ldrValue = analogRead(A0); // Read analog value from LDR  
    Serial.print("LDR Value: ");  
    Serial.println(ldrValue);  
    delay(500); // Delay for better readability  
}
```

Upload the code and open the **Serial Monitor** (115200 baud).

You will see the **light intensity value** changing when you cover or uncover the LDR.

Step 3: Connect the LED

Additional Component:

- 1x LED

Connections:

- LED Anode(+) → **D2 (GPIO 4)**
 - LED Cathode(-) → **GND**
-

Step 4: Automate LED Based on Light

Now we combine both – the LDR reads light levels and the LED turns ON/OFF based on it.

Final Code:

```
const int ledPin = D2;  
const int ldrPin = A0;  
  
void setup() {  
    pinMode(ledPin, OUTPUT);  
    Serial.begin(115200);  
}  
  
void loop() {  
    int ldrValue = analogRead(ldrPin);  
    Serial.print("LDR Value: ");  
    Serial.println(ldrValue);  
  
    if (ldrValue < 500) { // Dark environment
```

```
    digitalWrite(ledPin, HIGH); // Turn on LED
} else {
    digitalWrite(ledPin, LOW); // Turn off LED
}

delay(500);
}
```

Key Concepts Explained

- **LDR:** Sensor that detects light. Resistance decreases with more light.
 - **Voltage Divider:** Converts changing resistance into a voltage the ESP8266 can read.
 - **A0 Pin:** NodeMCU's analog input pin (reads values from 0-1023).
 - **LED Control:** LED turns on when light is low, turns off when it's bright.
-